

Capacitors and Inductors

Capacitor

- Stores charge and energy.

$$Q = CV$$

$$I = C \frac{dV}{dt}$$

- Energy:

$$U_C = \frac{1}{2} CV^2$$

- Energy density:

$$u_E = \frac{1}{2} \epsilon_0 E^2$$

Inductor

- Stores magnetic flux and energy.

$$N\Phi_B = LI$$

$$\mathcal{E} = -L \frac{dI}{dt}$$

- Energy:

$$U_L = \frac{1}{2} LI^2$$

- Energy density:

$$u_B = \frac{1}{2} \frac{B^2}{\mu_0}$$

Capacitors and Inductors in AC Circuits

Capacitor

$$V_{\max} = I_{\max} X_C$$

$$X_C = \frac{1}{\omega C}$$

- X_C = “capacitive reactance”
- Current leads voltage (ICE)

Inductor

$$V_{\max} = I_{\max} X_L$$

$$X_L = \omega L$$

- X_L = “inductive reactance”
- Current lags behind voltage (ELI)


Power

$$P = IV$$

Power dissipated by a resistor:



$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

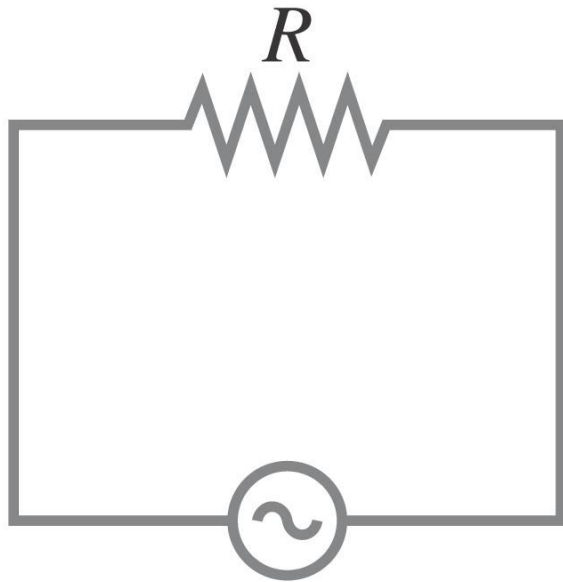

Power

$$V = IR$$

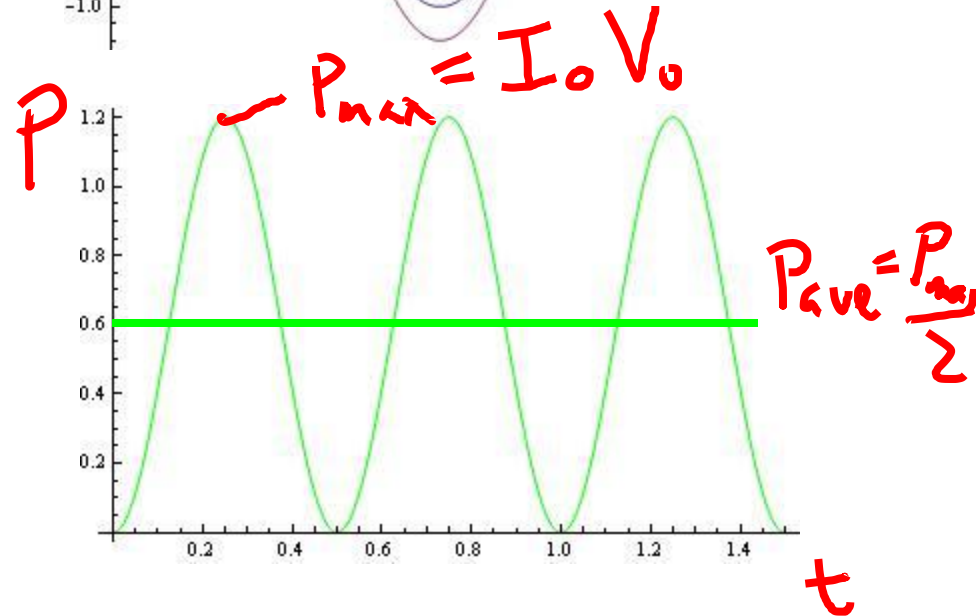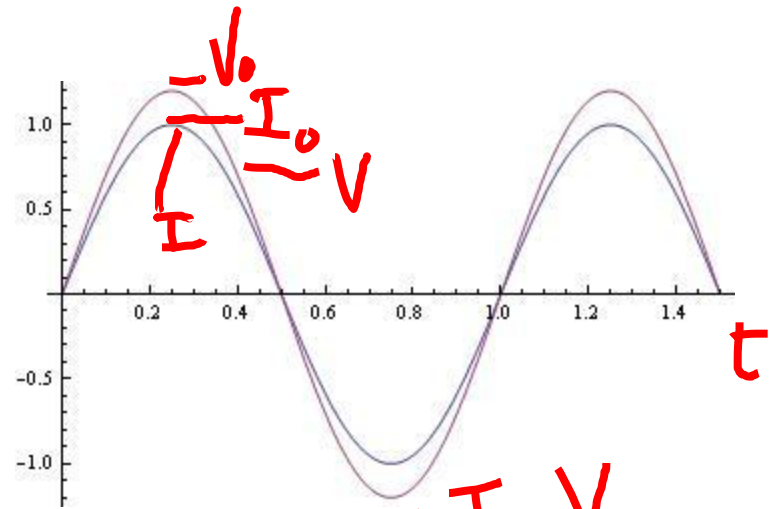

(a)

Figure 30.15a

Copyright © 2008 Pearson Education, Inc.

$$P_{ave} = \frac{1}{2} I_0 V_0$$

$$P_{ave} = I_{RMS} V_{RMS}$$

$$I_{RMS} = \frac{I_0}{\sqrt{2}}$$

$$V_{RMS} = \frac{V_0}{\sqrt{2}}$$

Power ICE

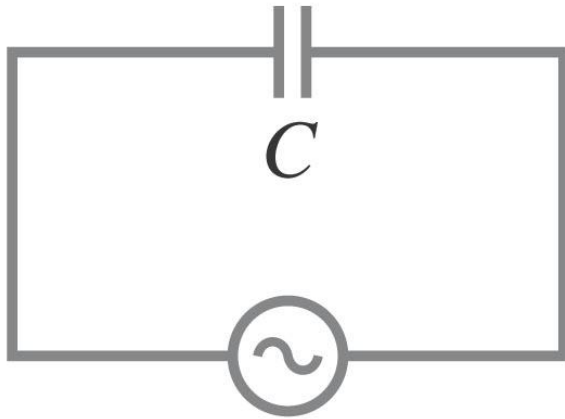



Figure 30.17a

(a)

Copyright © 2008 Pearson Education, Inc.

$$U_c = \frac{1}{2} CV^2$$

$$P_{ave} = 0$$

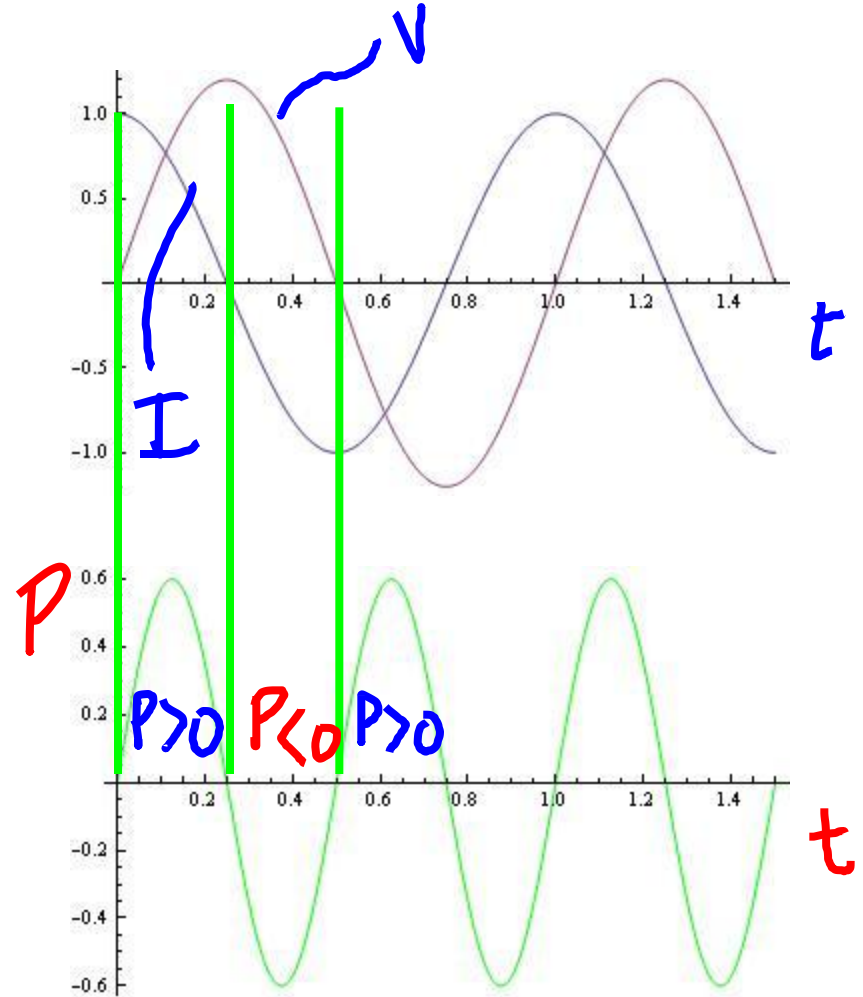

ELI

Power

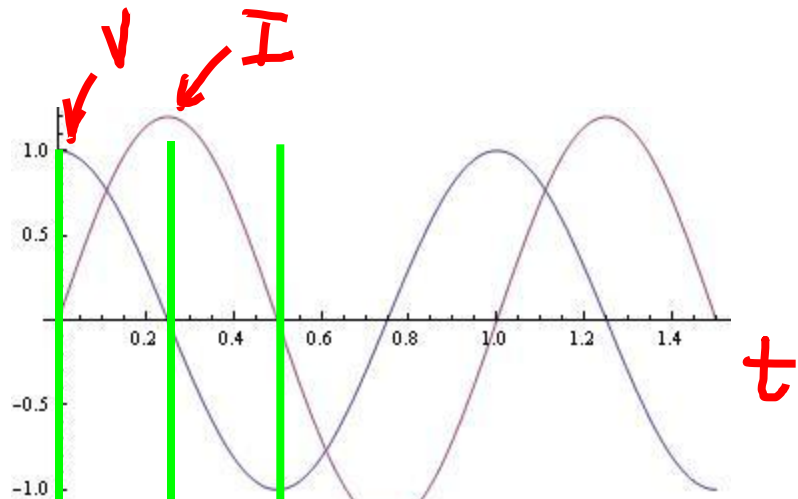
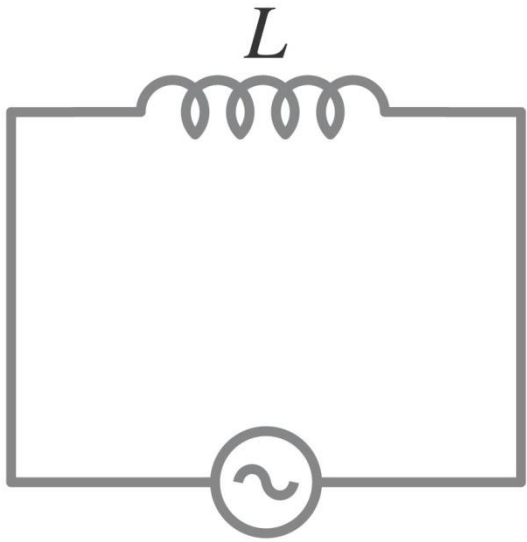



Figure 30.16a

Copyright © 2008 Pearson Education, Inc.

(a)

$$U_L = \frac{1}{2}LI^2$$

$$P_{ave} = 0$$

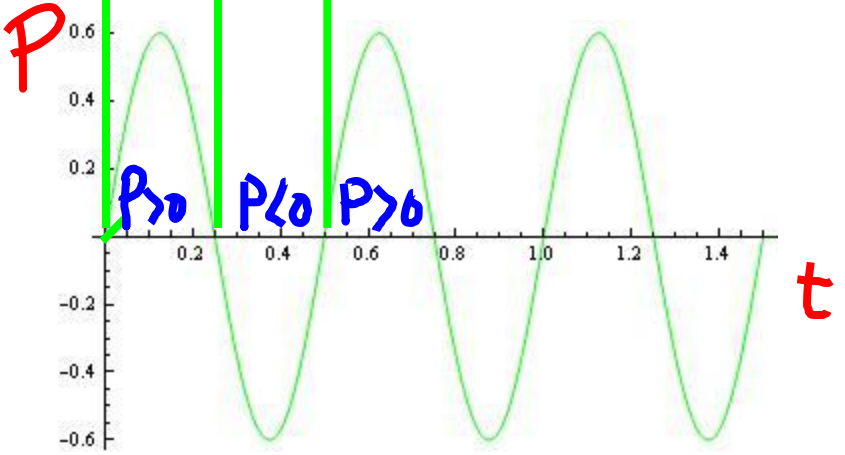

THE CIRC ^{VST} IS NOW COMPLETE



George Westinghouse

Thomas Edison

Nikola Tesla

Images from:


<http://www.movieposterdb.com/poster/ebdfeed0/>

<http://prweb.com>

http://en.wikipedia.org/wiki/Nikola_Tesla


<http://inventors.about.com/library/inventors/blwestinghouse.htm>

DC's Deficiency

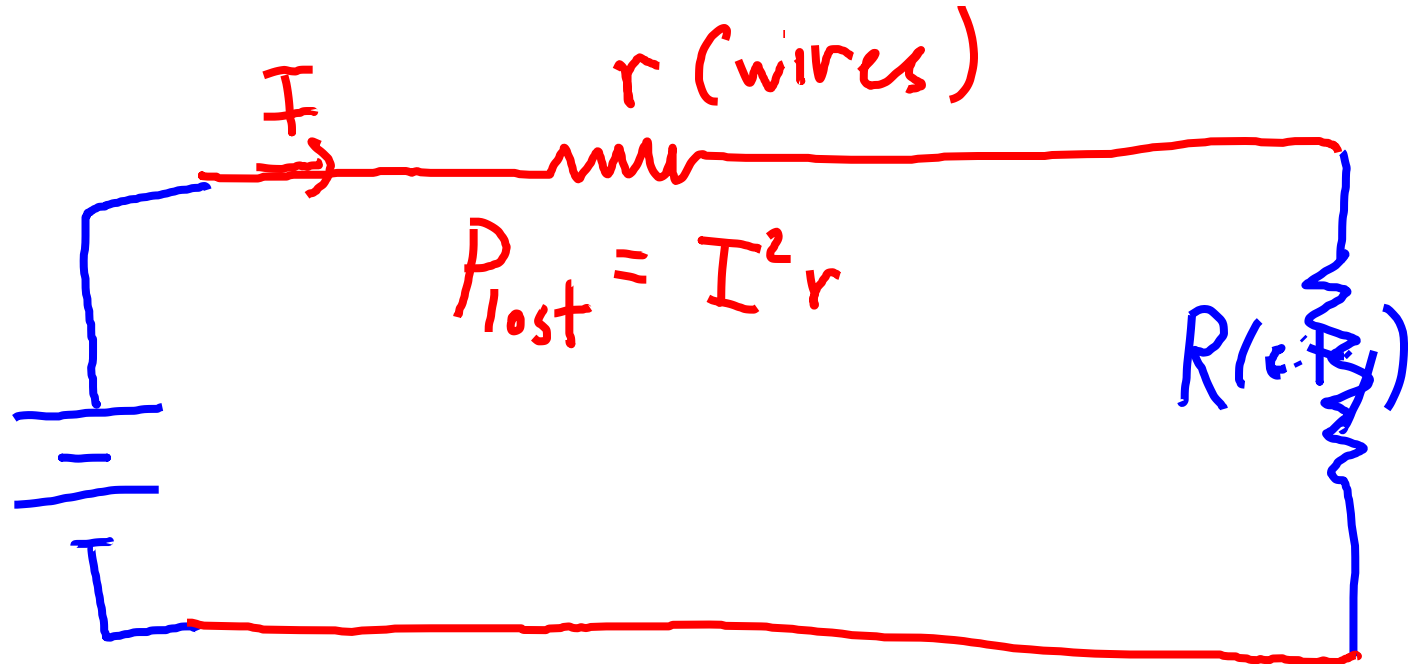

Mutual Inductance

- Emf will be induced in a coil when the flux through that coil is changing: $\mathcal{E} = -\frac{d}{dt} \int \vec{\mathbf{B}} \cdot \hat{\mathbf{n}} dA$
- That flux could be produced by current in a different coil: $B \propto I \Rightarrow \frac{dB}{dt} \propto \frac{dI}{dt}$
- So, a changing current in one coil, induces an emf in another coil: $\mathcal{E}_2 = M \frac{dI_1}{dt}$
- M = mutual inductance, a geometric and materials property.

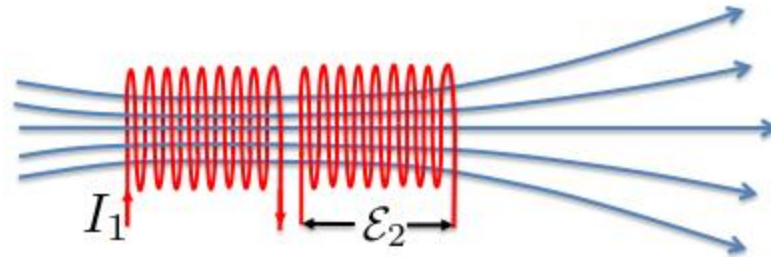

Transformer

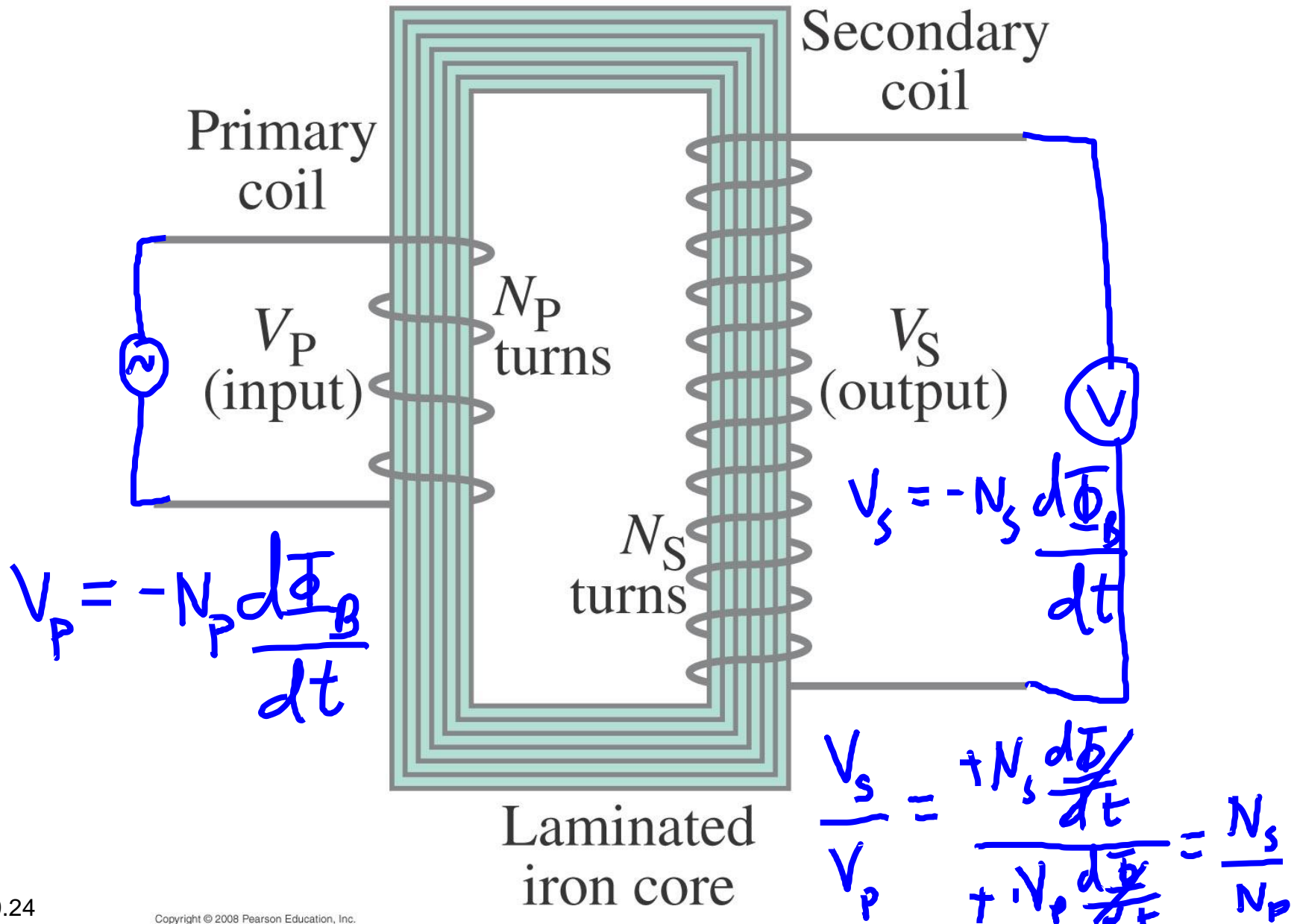


Figure 29.24

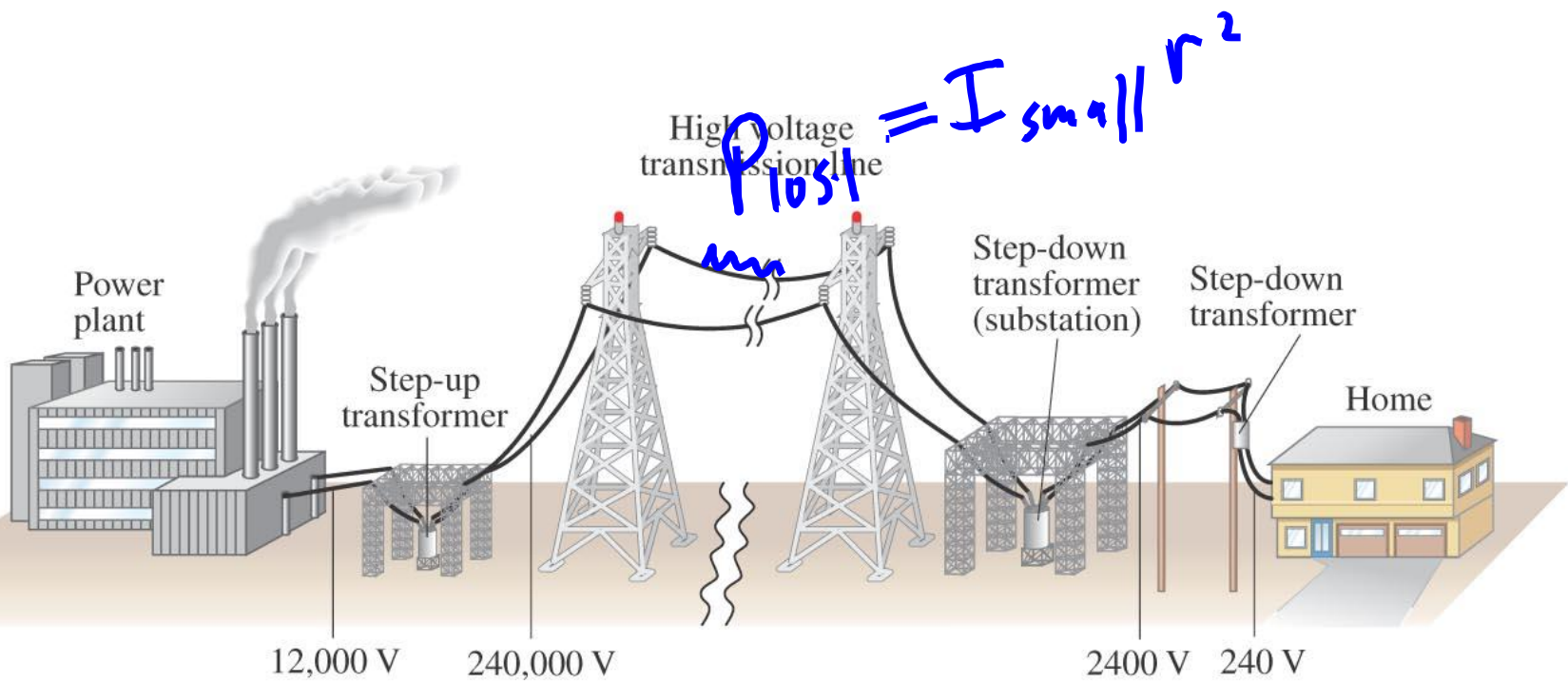


Figure 29.26

Copyright © 2008 Pearson Education, Inc.